


### Phys.G12-Q4W1-Electric Circuits-Test

#### Multiple Choice


Identify the choice that best completes the statement or answers the question.

Choose the best answer from the options that follow each question.

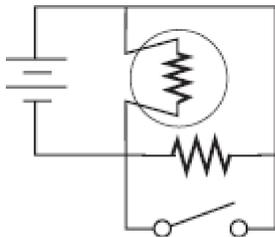- \_\_\_\_\_ 1. What happens when the switch is closed in the circuit shown below?




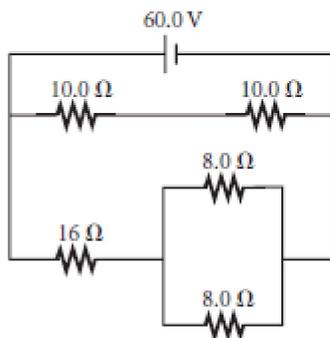- a. Current from the battery flows through the resistor.
  - b. The lamp goes out, because the battery terminals connect to each other.
  - c. Current from the battery flows through both the lamp and the resistor.
  - d. The lamp lights because current from the battery flows through the lamp.
- \_\_\_\_\_ 2. What is the equivalent resistance of the resistors in the figure shown below?



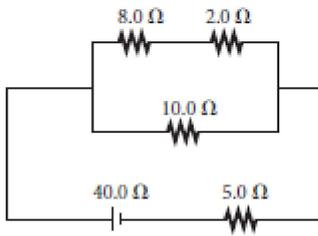- a.  $16 \Omega$
- b.  $18 \Omega$
- c.  $7.5 \Omega$
- d.  $10 \Omega$

- \_\_\_\_\_ 3. What is the equivalent resistance for the resistors in the figure shown below?



- 25  $\Omega$
- 7.5  $\Omega$
- 10.0  $\Omega$
- 5.0  $\Omega$


**Choose the best answer from the options that follow each question.**

- \_\_\_\_\_ 4. You have three 100  $\Omega$  resistors available. How would you connect these three resistors to produce a 150  $\Omega$  equivalent resistance? You must use all of the resistors.
- Connect one resistor in series with two resistors in parallel.
  - Connect all three resistors in series.
  - Connect all three resistors in parallel.
  - Connect two resistors in series with the third resistor in parallel to the first two.

**Choose the best answer from the options that follow each question.**

- \_\_\_\_\_ 5. Three resistors connected in parallel have potential differences across them labeled  $\Delta V_1$ ,  $\Delta V_2$ , and  $\Delta V_3$ . Which of the following expresses the potential difference across all three resistors?
- $\Delta V_t = \Delta V_1 = \Delta V_2 = \Delta V_3$
  - $\Delta V_t = \left( \frac{1}{\Delta V_1} + \frac{1}{\Delta V_2} + \frac{1}{\Delta V_3} \right)$
  - $\Delta V_t = \Delta V_1 + \Delta V_2 + \Delta V_3$
  - $\Delta V_t = \left( \frac{1}{\Delta V_1} + \frac{1}{\Delta V_2} + \frac{1}{\Delta V_3} \right)^{-1}$
- \_\_\_\_\_ 6. Three resistors with values of 3.0  $\Omega$ , 6.0  $\Omega$ , and 12  $\Omega$  are connected in parallel. What is the equivalent resistance of this combination?
- 0.26  $\Omega$
  - 33  $\Omega$
  - 1.7  $\Omega$
  - 9.0  $\Omega$

\_\_\_\_ 7.

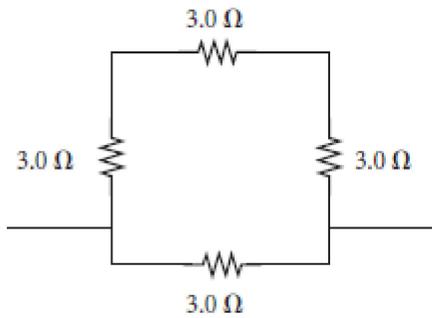


What is the equivalent resistance for the resistors in the figure shown above?

- a.  $2.2 \Omega$   
 b.  $3.0 \Omega$   
 c.  $1.3 \Omega$   
 d.  $0.75 \Omega$
- \_\_\_\_ 8. Three resistors connected in parallel carry currents labeled  $I_1$ ,  $I_2$ , and  $I_3$ . Which of the following expresses the total current  $I_t$  in the combined system?
- a.  $I_t = \left( \frac{1}{I_1} + \frac{1}{I_2} + \frac{1}{I_3} \right)$   
 b.  $I_t = I_1 + I_2 + I_3$   
 c.  $I_t = \left( \frac{1}{I_1} + \frac{1}{I_2} + \frac{1}{I_3} \right)^{-1}$   
 d.  $I_t = I_1 = I_2 = I_3$
- \_\_\_\_ 9. The equivalent resistance of a complex circuit is usually determined by
- a. adding and subtracting individual resistances.  
 b. inspection.  
 c. simplifying the circuit into groups of series and parallel circuits.  
 d. dividing the sum of the individual resistances by the number of resistances.

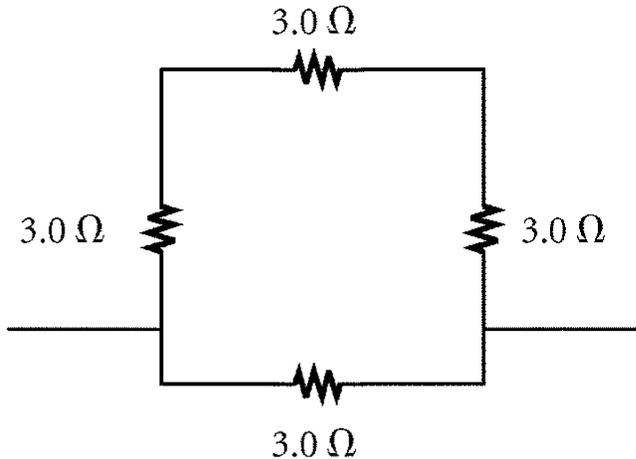**Choose the best answer from the options that follow each question.**

- \_\_\_\_ 10. The part of a circuit that converts electrical energy to other forms of energy is
- a. the load.  
 b. the switch.  
 c. a battery.  
 d. a wire.
- \_\_\_\_ 11. The equivalent resistance of a complex circuit is usually determined by
- a. simplifying the circuit into groups of series and parallel circuits.  
 b. adding and subtracting individual resistances.  
 c. dividing the sum of the individual resistances by the number of resistances.  
 d. inspection.

- \_\_\_\_\_ 12. To find the current in a complex circuit, it is necessary to know the
- number of branches in the circuit.
  - equivalent resistance of the circuit.
  - current in each device in the circuit.
  - potential difference in each device in the circuit.




- \_\_\_\_\_ 13. What is the equivalent resistance for the resistors in the figure shown above?
- |                 |                  |
|-----------------|------------------|
| a. $2.2 \Omega$ | c. $1.3 \Omega$  |
| b. $3.0 \Omega$ | d. $12.0 \Omega$ |

**Choose the best answer from the options that follow each question.**

- \_\_\_\_\_ 14. What distinguishes a parallel circuit from a series circuit?
- A parallel circuit always has more than one current path.
  - The equivalent resistance of a parallel circuit is less than that of a series circuit.
  - The voltage across the resistors in a parallel circuit is greater than it is in a series circuit.
  - The current in a parallel circuit is greater than in a series circuit.
- \_\_\_\_\_ 15. Four resistors having equal values are wired as a parallel circuit. How does the equivalent resistance of the circuit compare to the resistance of a single resistor?
- The equivalent resistance is greater than the resistance of any single resistor.
  - The equivalent resistance is one-fourth the resistance value of a single resistor.
  - The equivalent resistance is one-half the resistance value of a single resistor.
  - The equivalent resistance is the same as the resistance of any single resistor.
- \_\_\_\_\_ 16. Six resistors are wired in a parallel circuit. What is the voltage across each resistor in the circuit if the first resistor is connected to a 24 V battery?
- 24 V
  - 4 V
  - Voltage cannot be determined without the resistance values.
  - 0.25 V
- \_\_\_\_\_ 17. If the batteries in a portable CD player provide a terminal voltage of 12 V, what is the potential difference across the entire CD player?
- |          |          |
|----------|----------|
| a. 4.0 V | c. 3.0 V |
| b. 12 V  | d. 6.0 V |



\_\_\_ 25.

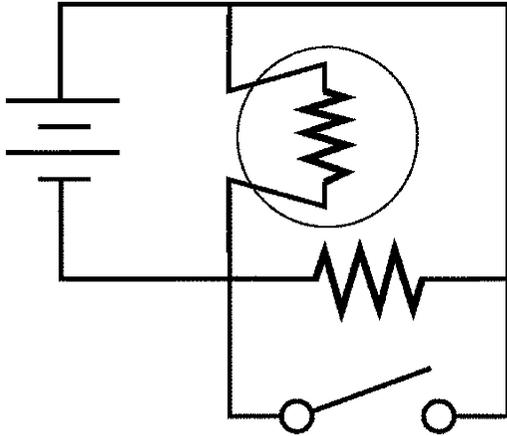

What happens when the switch is closed in the circuit shown above?

- a. The lamp lights because current from the battery flows through the lamp.
- b. Current from the battery is carried through both the lamp and the resistor.
- c. Current from the battery is carried through the resistor.
- d. The lamp goes out, because the battery terminals connect to each other.

=====